

Instructor: N. Chowdhury

October 1999


- Marks 1. The open-circuit characteristic data of a dc generator taken at 1200 r.p.m. are shown below:

Field current (A)	0.3	0.6	0.9	1.2	1.5	1.8	2.1	2.4	2.7	3.0
Term. voltage (V)	92	165	237	303	349	382	415	438	456	469

- 4 (a) The generator is connected in self-excited mode with an external rheostat connected in series with the field coil. Determine the no-load terminal voltage of the dc generator at 1200 r.p.m. if the field circuit resistance is adjusted to 180 ohms.
- 4 (b) Determine the no-load terminal voltage of the generator if the speed drops to 1100 r.p.m. All other conditions remain same as mentioned in (a).

Solution:

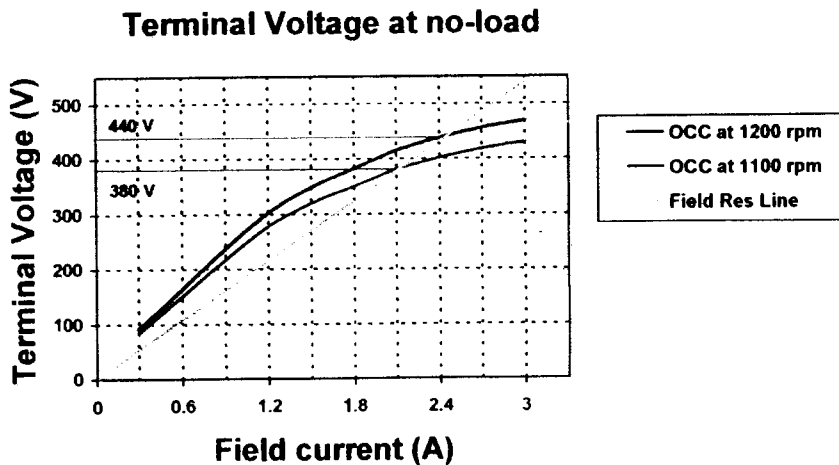- (a) At no-load the voltage drop,  $I_a R_a$ , is very small. Therefore, for all practical purposes  $V_t \approx E_a$ .  
Draw the OCC curve at 1200 rpm. Also draw the field circuit resistance line on the same graph.



The field circuit resistance is 180 ohms.  
Therefore, the no-load term

- (b) Draw a new OCC curve at 1100 rpm OCC data in the follow

For a given field current, the

$$E_a^{1100} = E_a^{1200} * \left( \frac{1100}{1200} \right)$$

The field circuit resistance line intersects the 1100 rpm OCC curve at 380 V (Figure 1).  
Therefore, the no-load terminal voltage at 1100 rpm is 380 V. Ans.

- 6 2. A dc shunt generator is driven at 900 r.p.m. with its output terminals connected to an electroplating process. The generator is delivering 180 A at a terminal voltage of 240 V. The field circuit resistance and the armature resistance of the generator are 60  $\Omega$  and 0.08  $\Omega$  respectively. Determine the output power of the generator. Determine the total electrical power generated by the dc machine.

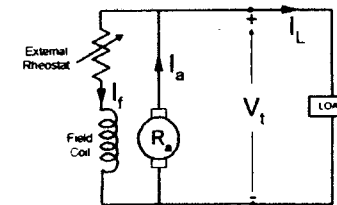


Figure 2. A dc shunt generator.

Solution:

$I_f = 180$  A and  $V_t = 240$  V. Field current,  $I_f = V_t / R_f$ .  $I_f = 240 / 60 = 4$  A

Armature current,  $I_a = I_L + I_f = 180 + 4 = 184$  A

The output power of this generator is:  $P_{out} = V_t \times I_L = 240 \times 180 = 43.2$  kW Ans.

The total power generated is given by:  $P_{total} = P_{out} + P_{loss}$  where  $P_{loss}$  is the power lost in the field and the armature circuit.

$$P_{total} = P_{out} + I_a^2 R_a + I_f^2 R_f$$

$$P_{total} = 43.2 \text{ kW} + (184)^2 (0.08) + (4)^2 (60)$$

$$P_{total} = 46868.5 \text{ W}$$

Total electrical power generated is 46868.5 W. Ans.

- 8 3. A 80-hp, 440-V, 500-rpm dc shunt motor has been purchased to drive a grinding machine at a cement factory. The motor is supplied from a 400 V dc supply and is drawing a line current of 120 A while driving the grinding machine at 470 r.p.m. The field circuit resistance and the armature resistance of the motor are

130  $\Omega$  and 0.05  $\Omega$  respectively. Determine the efficiency of the dc motor if the combined mechanical loss at 470 r.p.m. is 4 kW

Solution:

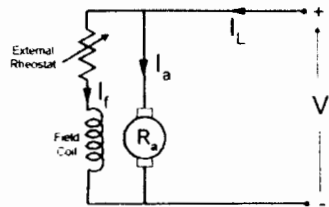


Figure 3. A dc shunt motor

Field current,  $I_f = V_t / R_f$ .  $V_t = 400$  V and  $R_f = 130 \Omega$ . Therefore,  $I_f = 400 / 130 = 3.08$  A  
Armature current,  $I_a = I_L - I_f = 120 - 3.08 = 116.92$  A

$$\begin{aligned} E_a &= V_t - I_a R_a \\ &= 400 - (116.92)(0.05) \\ &= 394.2 \text{ V} \end{aligned}$$

$$\begin{aligned} P_{out} &= P_e - \text{Rotational losses} \\ &= E_a I_a - 4 \text{ kW} \\ &= (394.2)(116.92) - 4 \text{ kW} \\ &= 42077 \text{ W} \end{aligned}$$

$$P_{in} = V_t I_L = (400)(120) = 48000 \text{ W}$$

$$\text{Efficiency} = P_{out} / P_{in} = 42077 / 48000 = 0.88 \text{ Ans.}$$

- 6 4. A dc series motor draws a line current of 160 A and runs at 500 r.p.m. at rated output when connected to a 480-V dc supply. The total resistance of the armature and the series field winding is 0.12 ohm. Determine the speed of the motor when the load changes so that it draws a line current of 120 A. Neglect saturation and armature reaction.

Solution:

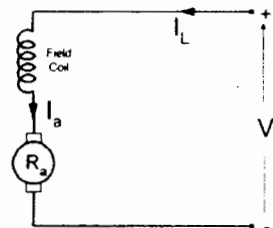


Figure 4. A dc series motor.

Calculate the counter emf at 500 rpm.

$$E_{a1} = V_t - I_{L1} (R_a + R_f) = 480 - (160)(0.12) = 460.8 \text{ V}$$

Calculate the counter emf for the second case

$$E_{a2} = V_t - I_{L2} (R_a + R_f) = 480 - (120)(0.12) = 465.6 \text{ V}$$

Neglecting saturation and armature reaction,  $E_a = K I_a \omega_m = K I_a \omega_m$

$$\frac{E_{a1}}{E_{a2}} = \frac{K I_{a1} \omega_{m1}}{K I_{a2} \omega_{m2}} = \frac{I_{a1} n_1}{I_{a2} n_2}$$

$$\frac{460.8}{465.6} = \frac{(160)(500)}{(120)n_2}$$

$$n_2 = \left( \frac{465.6}{460.8} \right) \left( \frac{160}{120} \right) 500$$

$$n_2 = 673.6 \text{ rpm Ans.}$$

THE END